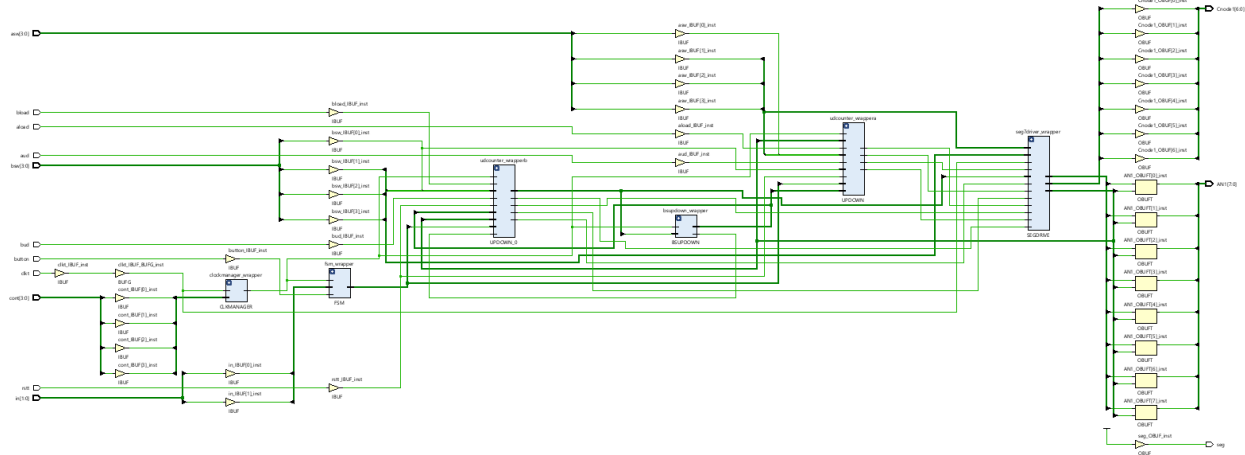


# ECE3300L Lab8 Group H Report (Sherwin Sathish & Mohamed Hamida)

## SCHEMATIC:



## Xdc for top.v:

```
## This file is a general .xdc for the Nexys A7-100T
## To use it in a project:
## - uncomment the lines corresponding to used pins
## - rename the used ports (in each line, after get_ports) according to the top level signal names in the project

## Clock signal
set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports { clk }]; # IO_L12P_T1_MRCC_35 Sch=clk100mhz
create_clock -add -name sys_clk_pin -period 10.00 -waveform { 0 5 } [get_ports { clk }];

##Switches
set_property -dict { PACKAGE_PIN J15      IOSTANDARD LVCMOS33 } [get_ports { asw[0] }]; #IO_L24N_T3_RS0_15 Sch=sw[0]
set_property -dict { PACKAGE_PIN L16      IOSTANDARD LVCMOS33 } [get_ports { asw[1] }]; #IO_L3N_T0_DQS_EMCCCLK_14
Sch=sw[1]
set_property -dict { PACKAGE_PIN M13      IOSTANDARD LVCMOS33 } [get_ports { asw[2] }]; #IO_L6N_T0_D08_VREF_14
Sch=sw[2]
set_property -dict { PACKAGE_PIN R15      IOSTANDARD LVCMOS33 } [get_ports { asw[3] }]; #IO_L13N_T2_MRCC_14 Sch=sw[3]
set_property -dict { PACKAGE_PIN R17      IOSTANDARD LVCMOS33 } [get_ports { bsw[0] }]; #IO_L12N_T1_MRCC_14 Sch=sw[4]
set_property -dict { PACKAGE_PIN T18      IOSTANDARD LVCMOS33 } [get_ports { bsw[1] }]; #IO_L7N_T1_D10_14 Sch=sw[5]
set_property -dict { PACKAGE_PIN U18      IOSTANDARD LVCMOS33 } [get_ports { bsw[2] }]; #IO_L17N_T2_A13_D29_14
Sch=sw[6]
set_property -dict { PACKAGE_PIN R13      IOSTANDARD LVCMOS33 } [get_ports { bsw[3] }]; #IO_L5N_T0_D07_14 Sch=sw[7]
set_property -dict { PACKAGE_PIN T8       IOSTANDARD LVCMOS18 } [get_ports { cont[0] }]; #IO_L24N_T3_34 Sch=sw[8]
set_property -dict { PACKAGE_PIN U8       IOSTANDARD LVCMOS18 } [get_ports { cont[1] }]; #IO_25_34 Sch=sw[9]
set_property -dict { PACKAGE_PIN R16      IOSTANDARD LVCMOS33 } [get_ports { cont[2] }]; #IO_L15P_T2_DQS_RDWR_B_14
Sch=sw[10]
set_property -dict { PACKAGE_PIN T13      IOSTANDARD LVCMOS33 } [get_ports { cont[3] }]; #IO_L23P_T3_A03_D19_14
Sch=sw[11]
set_property -dict { PACKAGE_PIN H6       IOSTANDARD LVCMOS33 } [get_ports { aud }]; #IO_L24P_T3_35 Sch=sw[12]
set_property -dict { PACKAGE_PIN U12      IOSTANDARD LVCMOS33 } [get_ports { bud }]; #IO_L20P_T3_A08_D24_14 Sch=sw[13]
set_property -dict { PACKAGE_PIN U11      IOSTANDARD LVCMOS33 } [get_ports { in[0] }]; #IO_L19N_T3_A09_D25_VREF_14
Sch=sw[14]
set_property -dict { PACKAGE_PIN V10      IOSTANDARD LVCMOS33 } [get_ports { in[1] }]; #IO_L21P_T3_DQS_14 Sch=sw[15]

## LEDs
set_property -dict { PACKAGE_PIN H17      IOSTANDARD LVCMOS33 } [get_ports { sumbit[0] }]; #IO_L18P_T2_A24_15
Sch=led[0]
set_property -dict { PACKAGE_PIN K15      IOSTANDARD LVCMOS33 } [get_ports { sumbit[1] }]; #IO_L24P_T3_RS1_15
Sch=led[1]
```

```

#set_property -dict { PACKAGE_PIN J13      IOSTANDARD LVCMOS33 } [get_ports { sumbit[2] }]; #IO_L17N_T2_A25_15
Sch=led[2]
#set_property -dict { PACKAGE_PIN N14      IOSTANDARD LVCMOS33 } [get_ports { sumbit[3] }]; #IO_L8P_T1_D11_14
Sch=led[3]
#set_property -dict { PACKAGE_PIN R18      IOSTANDARD LVCMOS33 } [get_ports { coutbit }]; #IO_L7P_T1_D09_14 Sch=led[4]
#set_property -dict { PACKAGE_PIN V17      IOSTANDARD LVCMOS33 } [get_ports { LED[5] }]; #IO_L18N_T2_A11_D27_14
Sch=led[5]
#set_property -dict { PACKAGE_PIN U17      IOSTANDARD LVCMOS33 } [get_ports { LED[6] }]; #IO_L17P_T2_A14_D30_14
Sch=led[6]
#set_property -dict { PACKAGE_PIN U16      IOSTANDARD LVCMOS33 } [get_ports { LED[7] }]; #IO_L18P_T2_A12_D28_14
Sch=led[7]
#set_property -dict { PACKAGE_PIN V16      IOSTANDARD LVCMOS33 } [get_ports { LED[8] }]; #IO_L16N_T2_A15_D31_14
Sch=led[8]
#set_property -dict { PACKAGE_PIN T15      IOSTANDARD LVCMOS33 } [get_ports { LED[9] }]; #IO_L14N_T2_SRCC_14
Sch=led[9]
#set_property -dict { PACKAGE_PIN U14      IOSTANDARD LVCMOS33 } [get_ports { LED[10] }]; #IO_L22P_T3_A05_D21_14
Sch=led[10]
#set_property -dict { PACKAGE_PIN T16      IOSTANDARD LVCMOS33 } [get_ports { LED[11] }];
#IO_L15N_T2_DQS_DOUT_CSO_B_14 Sch=led[11]
#set_property -dict { PACKAGE_PIN V15      IOSTANDARD LVCMOS33 } [get_ports { LED[12] }]; #IO_L16P_T2_CSI_B_14
Sch=led[12]
#set_property -dict { PACKAGE_PIN V14      IOSTANDARD LVCMOS33 } [get_ports { LED[13] }]; #IO_L22N_T3_A04_D20_14
Sch=led[13]
#set_property -dict { PACKAGE_PIN V12      IOSTANDARD LVCMOS33 } [get_ports { LED[14] }]; #IO_L20N_T3_A07_D23_14
Sch=led[14]
#set_property -dict { PACKAGE_PIN V11      IOSTANDARD LVCMOS33 } [get_ports { LED[15] }]; #IO_L21N_T3_DQS_A06_D22_14
Sch=led[15]

## RGB LEDs
#set_property -dict { PACKAGE_PIN R12      IOSTANDARD LVCMOS33 } [get_ports { LED16_B }]; #IO_L5P_T0_D06_14
Sch=led16_b
#set_property -dict { PACKAGE_PIN M16      IOSTANDARD LVCMOS33 } [get_ports { LED16_G }]; #IO_L10P_T1_D14_14
Sch=led16_g
#set_property -dict { PACKAGE_PIN N15      IOSTANDARD LVCMOS33 } [get_ports { LED16_R }]; #IO_L11P_T1_SRCC_14
Sch=led16_r
#set_property -dict { PACKAGE_PIN G14      IOSTANDARD LVCMOS33 } [get_ports { LED17_B }]; #IO_L15N_T2_DQS_ADV_B_15
Sch=led17_b
#set_property -dict { PACKAGE_PIN R11      IOSTANDARD LVCMOS33 } [get_ports { LED17_G }]; #IO_0_14 Sch=led17_g
#set_property -dict { PACKAGE_PIN N16      IOSTANDARD LVCMOS33 } [get_ports { LED17_R }]; #IO_L11N_T1_SRCC_14
Sch=led17_r

##7 segment display
set_property -dict { PACKAGE_PIN T10      IOSTANDARD LVCMOS33 } [get_ports { Cnode1[6] }]; #IO_L24N_T3_A00_D16_14
Sch=ca
set_property -dict { PACKAGE_PIN R10      IOSTANDARD LVCMOS33 } [get_ports { Cnode1[5] }]; #IO_25_14 Sch=cb
set_property -dict { PACKAGE_PIN K16      IOSTANDARD LVCMOS33 } [get_ports { Cnode1[4] }]; #IO_25_15 Sch=cc
set_property -dict { PACKAGE_PIN K13      IOSTANDARD LVCMOS33 } [get_ports { Cnode1[3] }]; #IO_L17P_T2_A26_15 Sch=cd
set_property -dict { PACKAGE_PIN P15      IOSTANDARD LVCMOS33 } [get_ports { Cnode1[2] }]; #IO_L13P_T2_MRCC_14 Sch=ce
set_property -dict { PACKAGE_PIN T11      IOSTANDARD LVCMOS33 } [get_ports { Cnode1[1] }]; #IO_L19P_T3_A10_D26_14
Sch=cf
set_property -dict { PACKAGE_PIN L18      IOSTANDARD LVCMOS33 } [get_ports { Cnode1[0] }]; #IO_L4P_T0_D04_14 Sch=cg
set_property -dict { PACKAGE_PIN H15      IOSTANDARD LVCMOS33 } [get_ports { seg }]; #IO_L19N_T3_A21_VREF_15 Sch=dp
set_property -dict { PACKAGE_PIN J17      IOSTANDARD LVCMOS33 } [get_ports { AN1[0] }]; #IO_L23P_T3_FOE_B_15 Sch=an[0]
set_property -dict { PACKAGE_PIN J18      IOSTANDARD LVCMOS33 } [get_ports { AN1[1] }]; #IO_L23N_T3_FWE_B_15 Sch=an[1]
set_property -dict { PACKAGE_PIN T9       IOSTANDARD LVCMOS33 } [get_ports { AN1[2] }]; #IO_L24P_T3_A01_D17_14
Sch=an[2]
set_property -dict { PACKAGE_PIN J14      IOSTANDARD LVCMOS33 } [get_ports { AN1[3] }]; #IO_L19P_T3_A22_15 Sch=an[3]
set_property -dict { PACKAGE_PIN P14      IOSTANDARD LVCMOS33 } [get_ports { AN1[4] }]; #IO_L8N_T1_D12_14 Sch=an[4]
set_property -dict { PACKAGE_PIN T14      IOSTANDARD LVCMOS33 } [get_ports { AN1[5] }]; #IO_L14P_T2_SRCC_14 Sch=an[5]
set_property -dict { PACKAGE_PIN K2       IOSTANDARD LVCMOS33 } [get_ports { AN1[6] }]; #IO_L23P_T3_35 Sch=an[6]
set_property -dict { PACKAGE_PIN U13      IOSTANDARD LVCMOS33 } [get_ports { AN1[7] }]; #IO_L23N_T3_A02_D18_14
Sch=an[7]

##Buttons
set_property -dict { PACKAGE_PIN C12      IOSTANDARD LVCMOS33 } [get_ports { rstt }]; #IO_L3P_T0_DQS_AD1P_15
Sch=cpu_resetrn
set_property -dict { PACKAGE_PIN N17      IOSTANDARD LVCMOS33 } [get_ports { aload }]; #IO_L9P_T1_DQS_14 Sch=btnc
set_property -dict { PACKAGE_PIN M18      IOSTANDARD LVCMOS33 } [get_ports { bload }]; #IO_L4N_T0_D05_14 Sch=btneu
set_property -dict { PACKAGE_PIN P17      IOSTANDARD LVCMOS33 } [get_ports { button }]; #IO_L12P_T1_MRCC_14 Sch=btnl
#set_property -dict { PACKAGE_PIN M17      IOSTANDARD LVCMOS33 } [get_ports { BTNR }]; #IO_L10N_T1_D15_14 Sch=btnr
#set_property -dict { PACKAGE_PIN P18      IOSTANDARD LVCMOS33 } [get_ports { BTND }]; #IO_L9N_T1_DQS_D13_14 Sch=btnd

```

## **Code Detail:**

```
`timescale 1ns / 1ps
```

```
module CLKMANAGER
```

```
(  
    input clk,  
    input rst,  
    input [3:0] SW,  
    output reg clkout =0  
);  
    reg [31:0] sel;
```

```
  
    wire [4:0] temp = {1'b1,SW};  
    always@(posedge clk or posedge rst)  
    begin: DREG  
        if(rst)  
            sel<= 32'd0;  
        else  
            sel<=sel+1;  
    end
```

```
always@(posedge clk)
```

```
begin
```

```
    case(SW)  
        5'd0: clkout <= sel[0];  
        5'd1: clkout <= sel[1];  
        5'd2: clkout <= sel[2];  
        5'd3: clkout <= sel[3];  
        5'd4: clkout <= sel[4];  
        5'd5: clkout <= sel[5];  
        5'd6: clkout <= sel[6];  
        5'd7: clkout <= sel[7];  
        5'd8: clkout <= sel[8];  
        5'd9: clkout <= sel[9];  
        5'd10: clkout <= sel[10];  
        5'd11: clkout <= sel[11];  
        5'd12: clkout <= sel[12];  
        5'd13: clkout <= sel[13];  
        5'd14: clkout <= sel[14];  
        5'd15: clkout <= sel[15];  
        5'd16: clkout <= sel[16];  
        5'd17: clkout <= sel[17];  
        5'd18: clkout <= sel[18];  
        5'd19: clkout <= sel[19];  
        5'd20: clkout <= sel[20];  
        5'd21: clkout <= sel[21];  
        5'd22: clkout <= sel[22];  
        5'd23: clkout <= sel[23];  
        5'd24: clkout <= sel[24];  
        5'd25: clkout <= sel[25];  
        5'd26: clkout <= sel[26];  
        5'd27: clkout <= sel[27];  
        5'd28: clkout <= sel[28];  
        5'd29: clkout <= sel[29];  
        5'd30: clkout <= sel[30];  
        5'd31: clkout <= sel[31];
```

```
    endcase
```

```
end
```

```
endmodule
```

The purpose of the clock manager is to have a counter and a 4-bit mux to output a clk with various levels of frequency depending on the integer div in this case. First we set up the counter by using an always loop that accounts for the reset, and sets up the different frequencies for all 16 values. Then we created an always loop that takes effect when the switches are changed, and we used a case statement for all 16 values of the 4-bit switches. Depending on the clkout that is selected by the switches, the frequency could vary for each clkout. We used the non-blocking assignment <= so that the code doesn't have to be done in order from top to bottom.

```
`timescale 1ns / 1ps
```

```
module UPDOWN(  
    input clk1,  
    input rst1,  
    input load,  
    input ud,  
    input [3:0] a,  
    output reg [3:0] tmp=0  
);  
  
always@(posedge clk1 or posedge rst1)  
begin  
    if(load)  
        begin  
            tmp=a;  
        end  
    else  
        begin  
            if(rst1)  
                begin  
                    if(ud)// 0 is up, 1 is down  
                        tmp<= 4'd9;  
                    else  
                        tmp<= 4'd0;  
                end  
            else  
                begin  
                    if(ud)  
                        if(tmp==4'd0)  
                            tmp <= 4'd9;  
                        else  
                            tmp <= tmp-1;  
                    else  
                        if(tmp==4'd9)  
                            tmp <= 4'd0;  
                        else  
                            tmp <= tmp+1;  
                    end  
                end  
            end  
        end  
    end  
end
```

```

endmodule
`timescale 1ns / 1ps
module UPDOWN_TB(
);
    reg clk_tb,rst_tb;
    reg l_tb;
    reg ud_tb;
    reg [3:0] atb;
    wire [3:0] cnt_tb;
    UPDOWN_COMP (
        .clk1(clk_tb),
        .rst1(rst_tb),
        .load(l_tb),
        .ud(ud_tb),
        .a(atb),
        .tmp(cnt_tb)
    );
    initial
        begin
            clk_tb = 0;
            rst_tb = 0;
            ud_tb = 0;
            l_tb = 1;
            atb = 3;
        end
    always
        begin
            #5 clk_tb = ~clk_tb;
        end
    always
        begin
            #20 l_tb = ~l_tb;
        end
endmodule

```

The purpose of this code is to count up or down in BCD. The always@(posedge or rst) was used because this is a sequential circuit, and the non-blocking assignment <= is used as well because this code runs in parallel. The if statement with en is used first because without the en the updown counter wouldn't run. Next there is a if statement to see if the reset value is 1, if it is then we need to see whether the updown counter is 0 for up or 1 for down. This is because if we are counting from 9 to 0 then the value should reset to 9, whereas if we count from 0 to 9 it should reset to 0.

```

`timescale 1ns / 1ps

```

```

module FSM(
    input [1:0] in,
    input but,
    input clk,
    output [1:0] outasm,
    output outsra,
    output outsrb
);

```

```

reg state;
reg [1:0] next_state;
reg [1:0] next_state2;

always@(posedge clk)
    if (but)
        state = ~state;
    else
        state = state;

always@(state)
case (state)
    1'b0://asm
        begin
            next_state = in;
        end
    1'b1://rot or shift for bar shift
        begin
            next_state2[0] = in[0];
            next_state2[1] = in[1];
        end
endcase
assign outasm = next_state;
assign outsra = next_state2[0];
assign outsrb = next_state2[1];
Endmodule
`timescale 1ns / 1ps

module FSM(
    input [1:0] in,
    input but,
    //input clk,
    output [1:0] outasm,
    output outsra,
    output outsrb
);

reg state;
reg [1:0] next_state;
reg [1:0] next_state2;

/* always@(posedge clk)
begin
    if (but)
        state = ~state;
    else
        state = state;
end*/
always@(but)
begin
case (but)
    1'b0://asm
        begin
            next_state = in;
        end
    1'b1://rot or shift for bar shift
        begin
            next_state2[0] = in[0];
            next_state2[1] = in[1];
        end
end

```

```

        endcase
    end
    assign outasm = next_state;
    assign outsra = next_state2[0];
    assign outsrb = next_state2[1];
endmodule

```

The fsm in this circuit passes either the add, subtract, multiply switches or the rotate and shift option for the barrel shifter will occur. The code is created so that when a button is pressed either one of these options will come to pass. This is to account for not enough I/O ports being available.

```
`timescale 1ns / 1ps
```

```

module BSUPDOWN(
    input clk1,
    output [1:0] s0,
    output [1:0] s1
);
    reg [3:0] tmp;
    always@(posedge clk1)
    begin
        tmp <= tmp+1;
    end
    assign s0[0] = tmp[0];
    assign s0[1] = tmp[2];
    assign s1[0] = tmp[1];
    assign s1[1] = tmp[3];
endmodule

```

The barrel shifter updown counter continuously counts up for a 4-bit number tmp and the digits are separated to equal different parts of s0 and s1 in the actual barrel shifter code to ensure randomization. The first and third digit of tmp go into the first barrel shifter as s0 and s1, the second and last digit go to the other barrel shifter for the same purpose.

```
`timescale 1ns / 1ps
```

```

module BARSHI(
    input [3:0] B,
    input [1:0] SW,
    input sel,
    output reg [3:0] P
);
    reg [3:0] sr;

    always@(*)
    begin

```

```

if(sel)
begin
case(SW) // rotate
    2'b00:
    begin
        sr[3]=B[3];
        sr[2]=B[2];
        sr[1]=B[1];
        sr[0]=B[0];
    end

    2'b01:
    begin
        sr[3]=B[0];
        sr[2]=B[3];
        sr[1]=B[2];
        sr[0]=B[1];
    end

    2'b10:
    begin
        sr[3]=B[1];
        sr[2]=B[0];
        sr[1]=B[3];
        sr[0]=B[2];
    end

    2'b11:
    begin
        sr[3]=B[2];
        sr[2]=B[1];
        sr[1]=B[0];
        sr[0]=B[3];
    end
endcase
end
else
begin//shift
case(SW)
    2'b00:
    begin
        sr[3]=B[3];
        sr[2]=B[2];
        sr[1]=B[1];
        sr[0]=B[0];
    end

    2'b01:
    begin
        sr[3]=0;
        sr[2]=B[3];
        sr[1]=B[2];
        sr[0]=B[1];
    end

```



```

        2'b10:
        begin
            sr[3]=0;
            sr[2]=0;
            sr[1]=B[3];
            sr[0]=B[2];
        end

        2'b11:
        begin
            sr[3]=0;
            sr[2]=0;
            sr[1]=0;
            sr[0]=B[3];
        end
    endcase
end
P = sr;
end
endmodule
`timescale 1ns / 1ps

module BARSHI_TB(
);
    reg [3:0] Btb;
    reg [1:0] SWtb;
    reg seltb;
    wire [3:0] Ptb;

    BARSHI COMP(
        .B(Btb),
        .SW(SWtb),
        .sel(seltb),
        .P(Ptb)
    );

    initial
    begin
        Btb = 7;
        SWtb = 2;
        seltb = 1;
    end
endmodule

```

For the barrel shifting code I created two separate cases to account for the option of shifting or rotating and the output is based on a two level 4 mux rows truth table. The 0 case represents rotation, while the 1 case represents shifting. The option to select is coming from the finite state machine in this case.

```
`timescale 1ns / 1ps
```

```
module ALU(  
    input [3:0] opa,  
    input [3:0] opb,  
    input [1:0] asm,  
    output [7:0] opc  
);  
    reg [7:0] ropc=0;  
    always@(*)  
    begin  
        case(asm)  
            2'b00:  
                begin  
                    ropc <= 0;  
                end  
  
            2'b01://ADD  
                begin  
                    ropc <= opa+opb;  
                end  
  
            2'b10://SUBTRACT  
                begin  
                    ropc = opa-opb;  
                end  
  
            2'b11: //MULTIPLICATION  
                begin  
                    ropc = opa * opb;  
                end  
  
        endcase  
    end  
    assign opc = ropc;  
endmodule  
`timescale 1ns / 1ps  
module alu_tb();  
    reg [3:0] opatb;  
    reg [3:0] opbtb;  
    reg [1:0] asmtb;  
  
    wire [7:0] opctb;  
  
    ALU alu_tb(  
        .opa(opatb),  
        .opb(opbtb),  
        .asm(asmtb),  
        //output to 7seg  
        .opc(opctb)  
    );  
    initial  
        begin: TEST
```

```

    asmtb = 3;
    opatb = 4;
    opbtb = 2;

    #100

    asmtb = 2;
    opatb = 4;
    opbtb = 4;

    #100

    asmtb = 1;
    opatb = 9;
    opbtb = 1;

    #100
    asmtb = 3;
    opatb = 1;
    opbtb = 9;
    #1000
    $finish;
end
endmodule

```

The alu code takes 2 single digit numbers and either adds, subtracts, or multiplies them to yield a 2 digit answer. This is a much simplified version because signs weren't necessary here, but there are 4 cases which depended on the asm chooser from the finite state machine. In addition to the add, subtract, and multiply options, there is also a null option if 00 is chosen from the two switches that control the operations.

```

`timescale 1ns / 1ps

module segdisplaydriver(
    input [31:0] inDigit,
    output reg [6:0] Cnode,
    output dp,
    output reg [7:0] AN,
    input nexysCLK, // 100MHz
    output reg divided_clk = 0 // 10kHz => 10ms period, 0.5ms ON, 0.5ms OFF
);
    reg [3:0] singledigit = 0;
    reg [3:0] refreshcounter = 0;
    // Calculate division value = 100MHz / (2 * desired frequency) - 1 => 10kHz => 4999

    localparam div_value = 25000;

    integer counter_value = 0;

```

```

always @(posedge nexysCLK)
begin
    if (counter_value == div_value) // For every (div_value) clock cycles, reset counter back to 0
        counter_value <= 0; // Use <= for parallel & same time, = for sequential - one after the other
    else
        counter_value <= counter_value + 1;
end

// divide clock
always @(posedge nexysCLK)
begin
    if (counter_value == div_value)
        divided_clk <= ~divided_clk; // Flip signal
    else
        divided_clk <= divided_clk; // Keep signal the same
end
/*CLOCK DIVIDER CODE*/

always @(posedge divided_clk)
begin
    refreshcounter <= refreshcounter + 1;
end

always @(refreshcounter)
begin
    case(refreshcounter)
        4'b0000: singledigit = inDigit[3:0]; // digit 1 value (right digit)
        4'b0001: singledigit = inDigit[7:4]; // digit 2 value
        4'b0010: singledigit = inDigit[11:8]; // digit 3 value
        4'b0011: singledigit = inDigit[15:12]; // digit 4 value
        4'b0101: singledigit = inDigit[19:16]; // digit 5 value missing 4'b0010
        4'b0110: singledigit = inDigit[23:20]; // digit 6 value
        4'b0111: singledigit = inDigit[27:24]; // digit 7 value
        4'b1000: singledigit = inDigit[31:28]; // digit 8 value (left digit)
    endcase
end

always @(refreshcounter)
begin
    case(refreshcounter)
        4'b0000: AN = 8'b11111110; // digit 1 ON (right digit)
        4'b0001: AN = 8'b11111101; // digit 2 ON
        4'b0010: AN = 8'b11111011; // digit 3 ON
        4'b0011: AN = 8'b11110111; // digit 4 ON
        4'b0100: AN = 8'b11101111; // digit 5 ON
        4'b0101: AN = 8'b11011111; // digit 6 ON
        4'b0110: AN = 8'b10111111; // digit 7 ON
        4'b0111: AN = 8'b01111111; // digit 8 ON (left digit)
        default: AN = 8'bZZZZZZZZ;
    endcase
end

assign dp = 1'b1;
always@(singledigit)

```

```

begin
  case (singledigit)
    4'd0: Cnode<= 7'b0000001; //0
    4'd1: Cnode<= 7'b1001111; //1
    4'd2: Cnode<= 7'b0010010; //2
    4'd3: Cnode<= 7'b0000110; //3
    4'd4: Cnode<= 7'b1001100; //4
    4'd5: Cnode<= 7'b0100100; //5
    4'd6: Cnode<= 7'b0100000; //6
    4'd7: Cnode<= 7'b0001111; //7
    4'd8: Cnode<= 7'b0000000; //8
    4'd9: Cnode<= 7'b0000100; //9
    4'd10:Cnode<= 7'b0001000; //A
    4'd11:Cnode<= 7'b1100000; //B
    4'd12:Cnode<= 7'b0110001; //C
    4'd13:Cnode<= 7'b1000010; //D
    4'd14:Cnode<= 7'b0110000; //E
    4'd15:Cnode<= 7'b0111000; //F
    default: Cnode = 7'b0000000; //DEFAULT CASE EVERYTHING ON
  endcase
end
endmodule

`timescale 1ns / 1ps

module SEGDRIVE_TB(

);
  reg [31:0] tmp_SW_tb;
  wire [6:0] Cnode_tb;
  wire dp_tb;
  wire [7:0] AN_tb;

  SEGDRIVE COMP (
    .tmp_SW(tmp_SW_tb),
    .Cnode(Cnode_tb),
    .dp(dp_tb),
    .AN(AN_tb)
  );

  initial
  begin
    //dp_tb = 1;
    tmp_SW_tb=0;
    #10
    tmp_SW_tb=4;
    #1000
    $finish;
  end

endmodule

```

This code takes an input of 32 switches and depending on when the switches change value, one of the many possible outputs will be selected to display on the 7 segment display. AN and dp are assigned in the beginning to make sure it is only one digit without the decimal place being shown. The different cases range from 0 to 9, and the 32-bit switch value selects the specific digit that needs to be modified. In this particular code 0 represents on, while 1 represents off.

```
`timescale 1ns / 1ps
```

```
module top(
    //INPUTS FROM FPGA
    input clkt,
    input rstt,
    input [3:0] asw,
    input [3:0] bsw,
    input [3:0] cont,
    input aud,
    input aload,
    input bud,
    input bload,
    input [1:0] in,
    input button,
    //OUTPUT TO 7SEG DISPLAY
    // output [7:0] opc,
    //output signc1,
    //7SEG DISPLAY INPUTS
    output [6:0] Cnode1,
    output [7:0] AN1,
    output seg
);

wire [31:0] seg7Digit;
//Send input changes to 7seg display
assign seg7Digit[3:0] = asw;
assign seg7Digit[7:4] = bsw;
// assign seg7Digit[11:8] = tmp_cnta;
//assign seg7Digit[19:16] = tmp_cntb;

wire [7:0] opc;

wire slowclk_out;
CLKMANAGER clockmanager_wrapper(
    .clk(clkt),
    .SW(cont),
    .clkout(slowclk_out)
);
//wire [3:0] tmp_cnta;
UPDOWN udcounter_wrappera(
    .rst1(rstt),
    .load(aload),
```

```

        .clk1(slowclk_out),
        .tmp(seg7Digit[11:8]),
        .a(asw),
        .ud(aud)
    );
//wire [3:0] tmp_cntb;
    UPDOWN udcounter_wrapperb(
        .rst1(rstt),
        .load(bload),
        .clk1(slowclk_out),
        .tmp(seg7Digit[19:16]),
        .a(bsw),
        .ud(bud)
    );
wire [1:0] sel1;
wire [1:0] sel2;
    BSUPDOWN bsupdown_wrapper(
        .clk1(slowclk_out),
        .s0(sel1),
        .s1(sel2)
    );
wire [1:0] amscon;
    FSM fsm_wrapper(
        .in(in),
        .but(button),
        .clk(slowclk_out),
        .outasm(amscon),
        .outsra(sra),
        .outsrb(srb)
    );
wire sra;
wire srb;
    BARSHI barshi_wrappera(
        .B(seg7Digit[11:8]),
        .SW(sel1),
        .sel(sra),
        .P(seg7Digit[15:12])
    );

    BARSHI barshi_wrapperb(
        .B(seg7Digit[19:16]),
        .SW(sel2),
        .sel(srb),
        .P(seg7Digit[23:20])
    );

    ALU alu_wrapper(
        .opa(seg7Digit[15:12]),
        .opb(seg7Digit[23:20]),
        .asm(asmcon),
        .opc(seg7Digit[31:24])
    );

```

```

SEGDRIVE seg7driver_wrapper(
    .nexysCLK(clkt),
    .inDigit(seg7Digit),
    .Cnode(Cnode1),
    .dp(seg),
    .AN(AN1)
);

```

```

endmodule

`timescale 1ns / 1ps
module top_tb();
    reg [3:0] opatb;
    reg [3:0] opbtb;
    reg audtb;
    reg budtb;
    reg altb;
    reg bltb;
    reg [1:0] asmtb;
    reg but1;
    reg clk_tb;

    wire [6:0] Cnode_tb;
    wire dp_tb;
    wire [7:0] AN_tb;

    top top_t(
        .clkt(clk_tb),
        .asw(opatb),
        .bsw(opbtb),
        .aud(audtb),
        .bud(budtb),
        .aload(altb),
        .bload(bltb),
        .in(asmtb),
        .button(but1),
        //output to 7seg
        .Cnode1(Cnode_tb),
        .seg(dp_tb),
        .AN1(AN_tb)
    );

    initial
        begin: TEST
            asmtb = 2;
            opatb = 4;
            opbtb = 2;
            audtb = 1;
            budtb = 1;
            but1 = 1;
            clk_tb=0;

```



```

#100

asmtb = 1;
opatb = 3;
opbtb = 6;
audtb = 0;
budtb = 1;
but1 = 0;
altb=1;
bltb=0;

#100

asmtb = 2;
opatb = 5;
opbtb = 2;
audtb = 1;
budtb = 0;
but1 = 1;

#100
asmtb = 3;
opatb = 8;
opbtb = 9;
audtb = 1;
budtb = 1;
but1 = 0;
#1000
$finish;
end

always
begin
#5 clk_tb = ~clk_tb;
end

endmodule

```

The top file basically instantiates all the previous files and establishes connections to make the circuit display the desired results. So initially the output of the clock manager goes to the two updown counters that were instantiated, the finite state machine that was created, and the upcounter that connects to the s0 and s1 of the two barrel shifters that were created. This is to ensure a synchronous clock for the entire circuit. The output of the updowns connect to the barrel shifters as well as the 7-seg display, and the output of the barrel shifters connect to the two input digits of the alu as well as the 7-seg display. To take care of this a 32-bit wire is created and specific indexes can be addressed like seg7digit[23:20]. This allows one output to go two places through wiring. From the barrel shifter updown counter, the first and third digit of tmp go into the first barrel shifter as s0 and s1, the second and last digit go to the other barrel shifter for the same purpose. The fsm in this circuit passes either the add, subtract, multiply

switches or the rotate and shift option for the barrel shifter will occur. The seg7Digit wire establishes most of the connections described, while also displaying the interconnections on the 7-seg display.

### **Corner Cases/Error :**


*One corner case can be A-D can be displayed, to cope this either the default case in the case statements should be 9, or the user simply just shouldn't input those values.*

*Another corner case can be the CLKMANAGER Testbench. At first the testbench wasn't working because of :*

*always@(SW)  
begin*

*The problem is that the loop can only run if the SW changes, so we had to change SW to posedge clk or posedge rst, so that the code could effectively work in the testbench.*
 
### **IMPLEMENTED DESIGN/ TIMING SUMMARY:**



### Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 5.507 ns	Worst Hold Slack (WHS): 0.263 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 80	Total Number of Endpoints: 80	Total Number of Endpoints: 50
All user specified timing constraints are met.		


### POWER SUMMARY:

#### Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

<b>Total On-Chip Power:</b>	<b>0.113 W</b>
<b>Design Power Budget:</b>	<b>Not Specified</b>
<b>Power Budget Margin:</b>	<b>N/A</b>
<b>Junction Temperature:</b>	<b>25.5°C</b>
Thermal Margin:	59.5°C (12.9 W)
Effective $\theta_{JA}$ :	4.6°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low
<a href="#">Launch Power Constraint Advisor</a> to find and fix invalid switching activity	

#### On-Chip Power

 

### UTILIZATION:

Name	Slice LUTs (63400)	Slice Registers (126800)	F7 Muxes (31700)	F8 Muxes (15850)	Slice (15850)	LUT as Logic (63400)	Bonded IOB (210)	BUFGCTRL (32)
▼ N top	65	72	2	1	35	65	37	1
bsupdown_wrapper (BSUPDOWN)	3	4	0	0	2	3	0	0
clockmanager_wrapper (CLKMANAGER)	5	16	2	1	5	5	0	0
fsm_wrapper (FSM)	1	3	0	0	2	1	0	0
seg7driver_wrapper (SEGDRIVE)	26	41	0	0	23	26	0	0
udcounter_wrappera (UPDOWN)	15	4	0	0	5	15	0	0
udcounter_wrapperb (UPDOWN_0)	15	4	0	0	7	15	0	0

**RESOURCE USAGE:**

WNS	TNS	WHS	THS	WBSS	TPWS	Total Power	Failed Routes	LUT	FF
								65	66
5.507	0.000	0.263	0.000		0.000	0.113	0	65	66